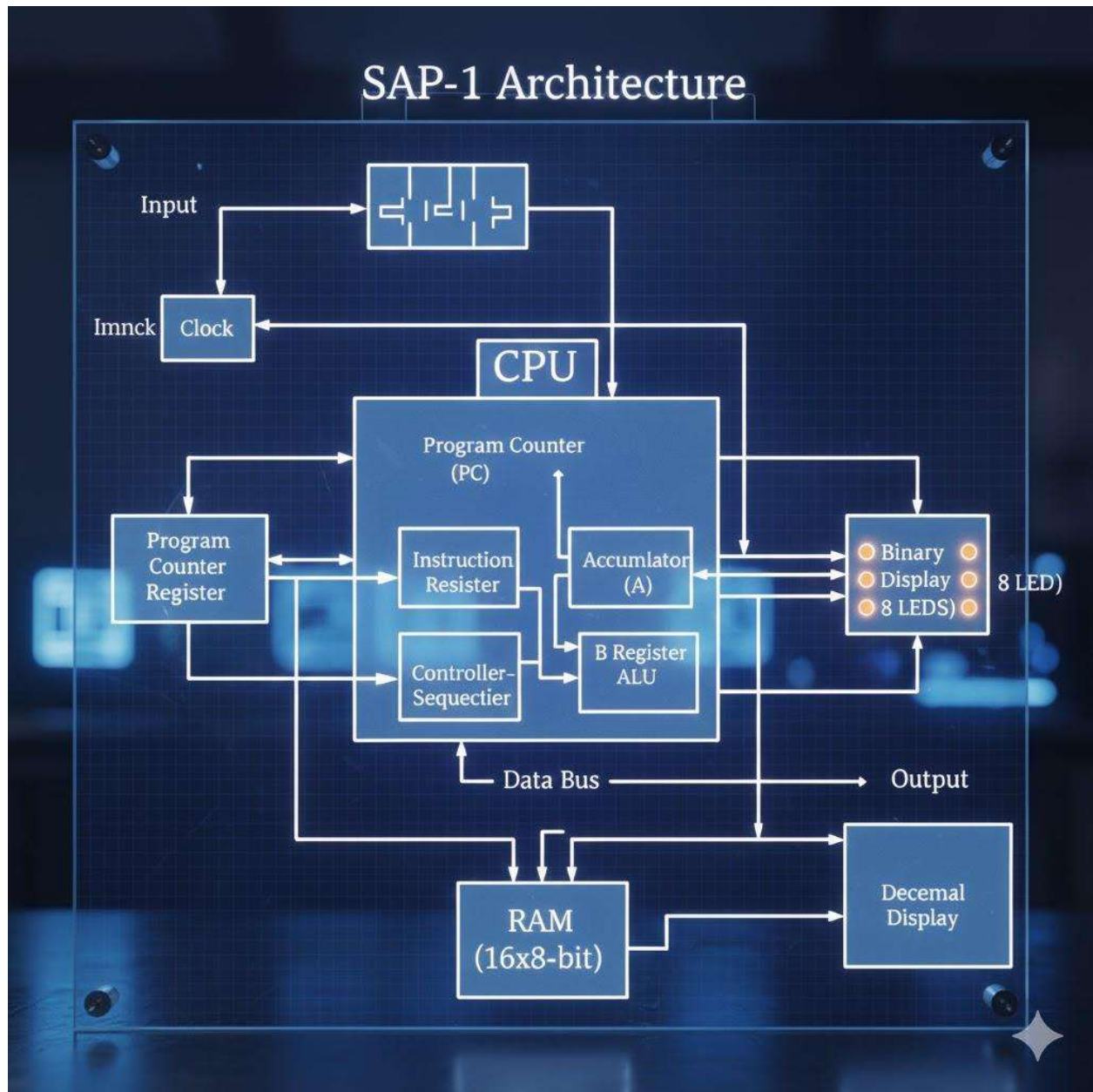


The SAP-1 Architecture



- Prepared By: Mahmoud Saleh Elsayed

1. Introduction

The Simple-As-Possible computer, Model 1 (SAP-1), is an educational, bus-organized processor designed to illustrate the Von-Neumann architecture and the fundamental fetch-execute cycle. It operates using an 8-bit data bus and a limited instruction set, providing a clear, step-by-step model of how a Central Processing Unit (CPU) interacts with memory and performs arithmetic logic operations.

The SAP-1 serves as a conceptual blueprint, simplifying the operation of a full-scale computer into ten main components interconnected by the central bus. Its simplicity ensures an in-depth understanding of the control logic and timing signals required for the stored-program concept.

2. Functional Components and Their Roles

The architecture relies on an 8-bit **W-Bus** for inter-component data transfer, regulated by tri-state buffers to ensure only one component drives the bus at any given clock cycle.

The ten main components and their primary roles are:

- **Program Counter (PC)**: A 4-bit counter (**Counter2**) that holds the memory address of the next instruction to be fetched. It is incremented ($\$W_{\text{C}}_W_{\text{p}}\$$ signal) after each instruction fetch.
- **Memory Address Register (MAR)**: A 4-bit register (**Register - 4 bits**) that stores the memory address (either from the PC or the Instruction Register) required to access the RAM.
- **RAM**: The memory unit (**RAM 16x8**) that stores both program instructions and data (emulating the Von-Neumann model).
- **Instruction Register (IR)**: An 8-bit register (**Register**) that stores the fetched instruction. The upper 4 bits are the **Opcode** (for the Control Unit), and the lower 4 bits are the **Operand** (a memory address).
- **Controller/Sequencer (CU)**: The control logic (**Controller**) that generates the necessary 12 control signals (micro-instructions, like $\$W_{\text{L}}_W_{\text{a}}\$$, $\$W_{\text{E}}_W_{\text{p}}\$$) to coordinate the entire operation in sync with the clock.
- **Accumulator (Reg A)**: An 8-bit register (**Register**) that acts as the primary operand for the ALU and stores intermediate results.
- **B Register (Reg B)**: An 8-bit buffer register (**Register**) that holds the second operand for ALU operations.
- **Adder/Subtractor (ALU)**: The arithmetic logic unit (**ALU**, constructed from **FA/One/ZeroCircuit** sub-circuits) that performs 8-bit addition and subtraction (using two's complement) on the contents of Reg A and Reg B.
- **Output Register (OUT)**: An 8-bit register (**Register**) that latches the final result from the bus for display.

3. Step-by-Step Operation

The SAP-1 executes a program through a repetitive **Instruction Cycle**, which is divided into a **Fetch Phase** and an **Execute Phase**, coordinated by the Control Unit's internal ring counter (T0–T5).

1. The Fetch Phase (T0, T1, T2)

This phase retrieves the next instruction from memory and loads it into the Instruction Register.

- **T0 (Address Transfer):** The Program Counter (\$Wtext{PC}\$) places the address onto the W-Bus using the \$Wtext{E}_Wtext{p}\$ signal. The Memory Address Register (\$Wtext{MAR}\$) simultaneously loads this address using the \$Wtext{L}_Wtext{m}\$ signal.
- **T1 (PC Increment):** The PC is synchronously incremented using the \$Wtext{C}_Wtext{p}\$ signal, preparing for the next instruction address.
- **T2 (Instruction Load):** The 8-bit instruction is fetched from RAM (addressed by MAR) and placed onto the W-Bus via the \$Wtext{C}_Wtext{E}\$ signal. The Instruction Register (\$Wtext{IR}\$) loads the instruction using the \$Wtext{L}_Wtext{i}\$ signal.

2. The Decode and Execute Phase (T3, T4, T5)

The Opcode (upper 4 bits) of the instruction in the IR is sent to the Control Unit, which decodes it to determine the required micro-instructions for the execution phase.